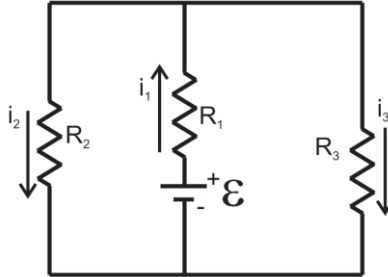


## Theory

Consider the following circuit: (Note that the directions for the currents have been chosen for you.) The following are the predicted values for your circuit elements:  $\epsilon = 5.0 \text{ V}$ ,  $R_1 = 50.0 \Omega$ ,  $R_2 = 60.0 \Omega$ ,  $R_3 = 300.0 \Omega$ .



- Predict the equivalent resistance and record it in the table (make your own in excel).
- Using Kirchhoff's laws, find the currents:  $i_1$ ,  $i_2$ , and  $i_3$ . Record your predicted currents in the data table, along with the predicted resistance and voltage values.
- Use the predicted currents above to calculate the predicted power lost by each resistor and the power supplied by the battery.

## Experiment

Verify that your circuit is setup properly on the breadboard.

- You should measure each resistor's actual resistance, and the equivalent resistance and put that in your data table. Measure resistance using the  $\Omega$  setting (for individual resistances you must take the resistor out of the circuit).
- Measure the voltage across the power supply and record that as well, using the  $\overline{\overline{V}}$  setting.
- Next measure each current. In order to measure the current you will have to move the red lead to the port with an **A**. The multimeter will need to be in the  $\overline{\overline{A}}$  mode, AND more importantly you need to "break" open the circuit and insert the multimeter in series at the location you wish to measure the current.
- Calculate the powers, and fill in the table. Check that the power dissipated by resistors is equal to the power supplied by the battery.
- Calculate percent difference:  $\frac{|measured - predicted|}{predicted} \times 100\%$

**Data Table**

	Predicted ( $\Omega$ )	Measured ( $\Omega$ )	%Difference
$R_1$	50		
$R_2$	60		
$R_3$	300		
$R_{eq}$			
	Predicted (V)	Measured (V)	%Difference
$\mathcal{E}$	5		
	Predicted (A)	Measured (A)	%Difference
$i_1$			
$i_2$			
$i_3$			
	Predicted (W)	Measured (W)	%Difference
$P_{R1}$			
$P_{R2}$			
$P_{R3}$			
$P_{\mathcal{E}}$			